

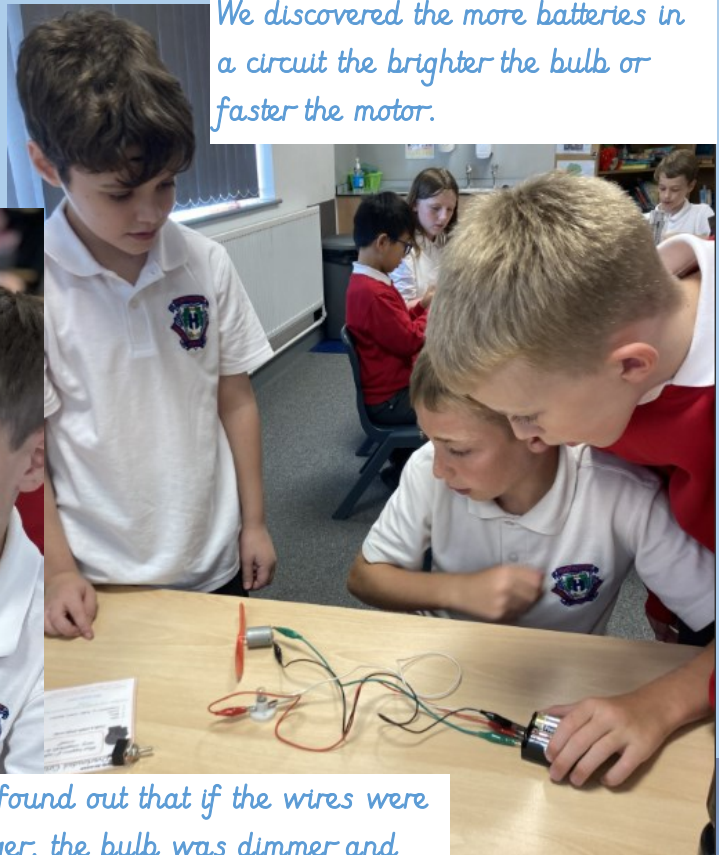


Electricity Challenge Stations

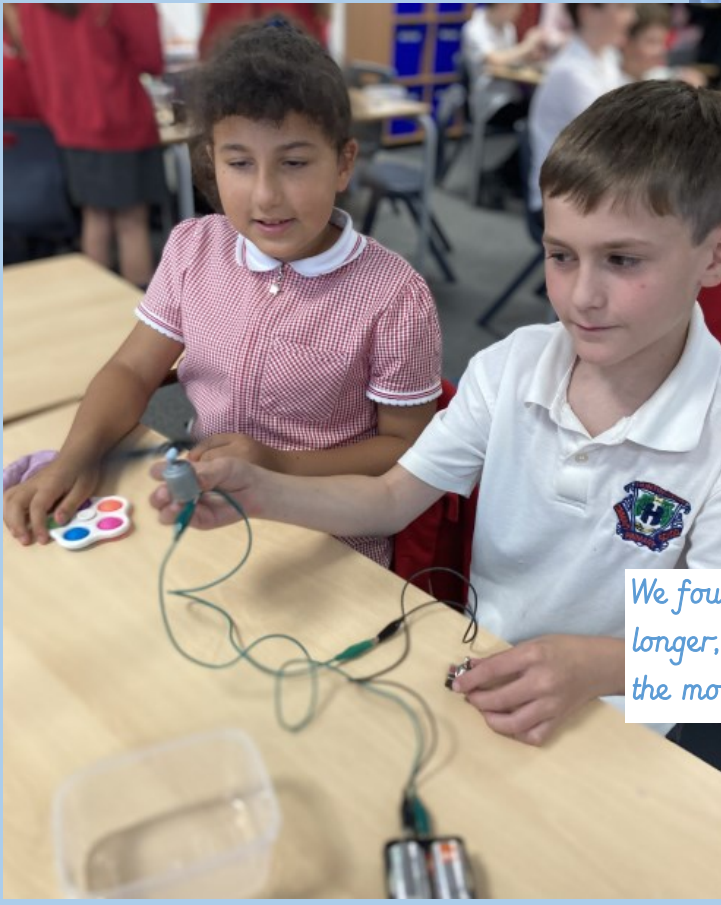We discovered the more batteries in a circuit the brighter the bulb or faster the motor.



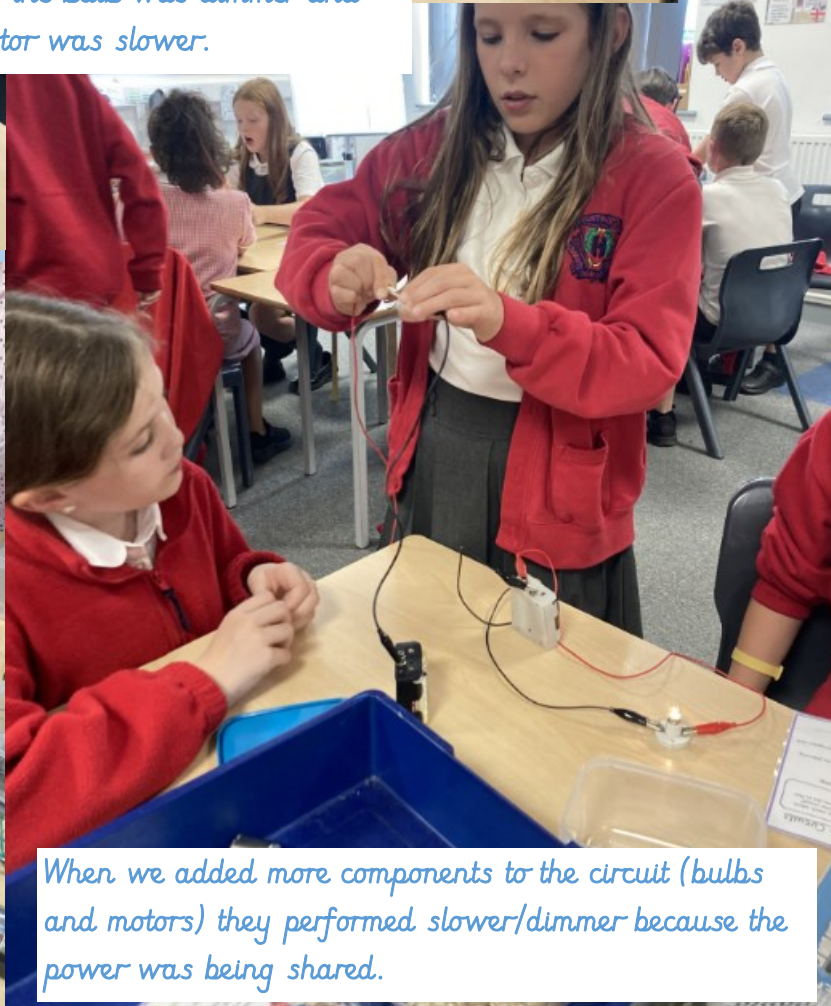We found out that if the wires were longer, the bulb was dimmer and the motor was slower.



When we added more components to the circuit (bulbs and motors) they performed slower/dimmer because the power was being shared.